

Electronics

JEST-2012

- Q1. The ratio of maximum to minimum resistance that can be obtained with N $1\text{-}\Omega$ resistors is
(a) N (b) N^2 (c) 1 (d) ∞

Ans.: (b)

Solution: Resistance in series is maximum and minimum in parallel combination


$$R_s = 1+1+1+1+\dots N = N$$

$$\frac{1}{R_p} = \frac{1}{1} + \frac{1}{1} + \frac{1}{1} + \frac{1}{1} + \frac{1}{1} + \dots = N$$

$$\frac{R_s}{R_p} = N \times N = N^2$$


- Q2. The net charge of an n -type semiconductor is
(a) positive (b) zero (c) negative (d) dependent

Ans.: (b)

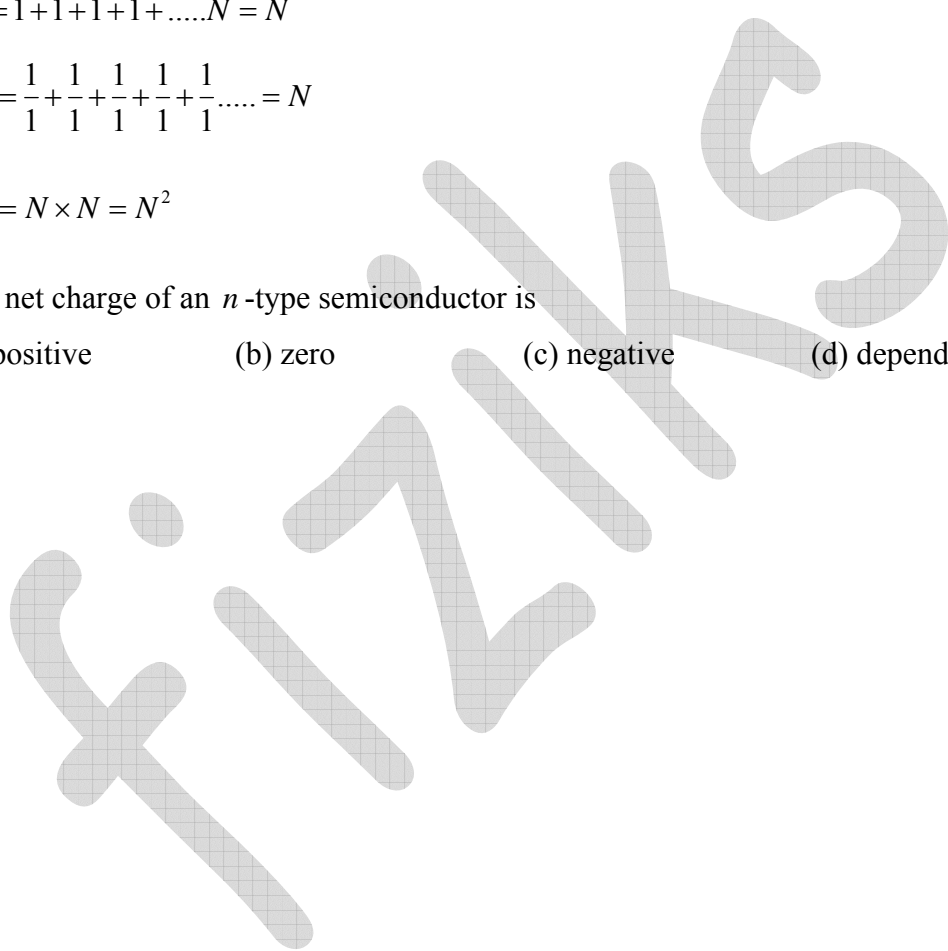





JEST-2014

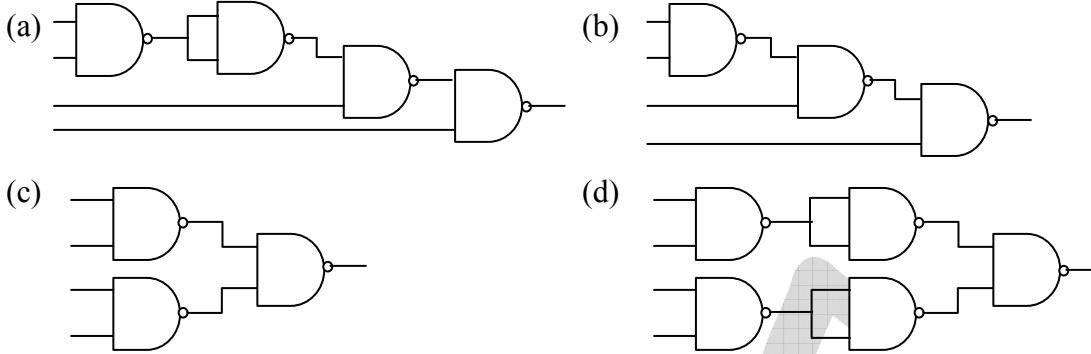Q3. Which of the following circuits will act like a 4-input NAND gate?



Ans.: (d)

Solution:

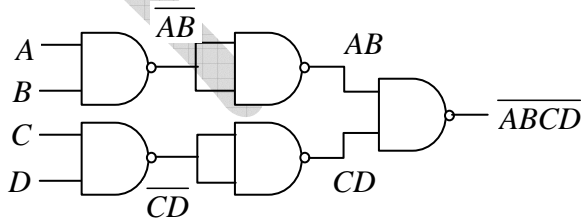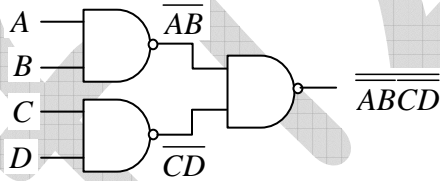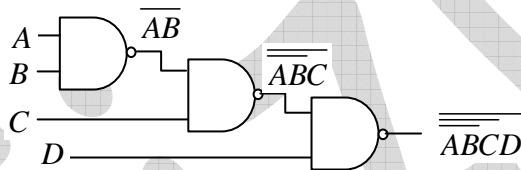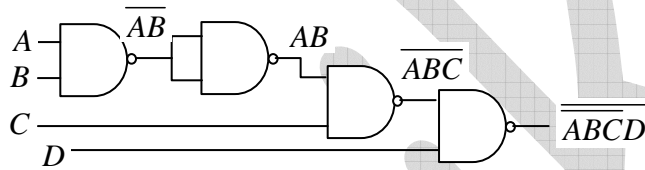

Q4. The formula for normal strain in a longitudinal bar is given by $\varepsilon = \frac{F}{AE}$, where F is normal force applied, A is cross-sectional area of the bar and E is Young's modulus. If $F = 50 \pm 0.5N$, $A = 0.2 \pm 0.002m^2$ and $E = 210 \times 10^9 \pm 1 \times 10^9$ Pa, the maximum error in the measurement of strain is

- (a) 1.0×10^{-12} (b) 2.95×10^{-11} (c) 1.22×10^{-9} (d) 1.19×10^{-9}

Ans.: (b)

Solution: $\varepsilon = \frac{F}{AE} \Rightarrow \frac{\Delta\varepsilon}{\varepsilon} = \frac{\Delta F}{F} + \frac{\Delta A}{A} + \frac{\Delta E}{E} = \frac{0.5}{50} + \frac{0.002}{0.2} + \frac{1 \times 10^9}{210 \times 10^9}$

$$\frac{\Delta\varepsilon}{\varepsilon} = 0.02476 \Rightarrow \Delta\varepsilon = 0.02476 \times \varepsilon = \frac{0.02476 \times 50}{0.2 \times 210 \times 10^9} = 2.95 \times 10^{-11}$$

Q5. A 100 ohms resistor carrying current of 1 Amp is maintained at a constant temperature of $30^\circ C$ by a heat bath. What is the rate of entropy increase of the resistor?

- (a) 3.3 Joules/K/sec (b) 6.6 Joules/K/sec
(c) 0.33 Joules/K/sec (d) None of the above


Ans.: (c)

Solution: $W = qV \Rightarrow W = itV \Rightarrow W = i^2 R t$. Now, $\frac{\partial W}{\partial T} = \frac{i^2 R t}{T} = \frac{1 \times 100}{30 + 273} = 0.33$

JEST-2015

Q6. What is the voltage at the output of the following operational amplifier circuit. [See in the figure]?

- (a) 1V
- (b) 1mV
- (c) 1μV
- (d) 1nV

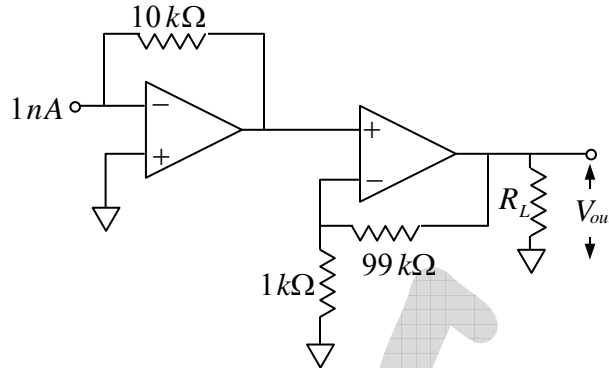

Ans.: (b)

Solution: Output of first Op-Amp $v_{o1} = -(10 \times 10^3)(1 \times 10^{-9}) = -10^{-5}$ volt

Output of first Op-Amp $v_{out} = \left(1 + \frac{99}{1}\right) \times 10^{-5} = 10^{-3}$ volts = 1mV

Q7. The reference voltage of an analog to digital converter is 1 V . The smallest voltage step that the converter can record using a 12-bit converter is,

- (a) 0.24V
- (b) 0.24mV
- (c) 0.24μV
- (d) 0.24nV

Ans.: (b)

Solution: Smallest voltage step = $\frac{1}{2^{12}-1} \approx 0.24$ mV

Q8. In Millikan's oil drop experiment the electronic charge e could be written as $k\eta^{1.5}$, where k is a function of all experimental parameters with negligible error. If the viscosity of air η is taken to be 0.4% lower than the actual value, what would be the error in the calculated value of e ?

- (a) 1.5%
- (b) 0.7%
- (c) 0.6%
- (d) 0.4%

Ans.: (d)

Solution: Electronic charge is proportional to the viscosity i.e. $e = k\eta^{1.5} = k\eta^{3/2}$

Now error in the measurement of charge is $\sigma_e^2 = \left(\frac{\partial e}{\partial \eta}\right)^2 \sigma_\eta^2$

$\Rightarrow \sigma_e = \left(\frac{\partial e}{\partial \eta}\right) \sigma_\eta$, where $\frac{\partial e}{\partial \eta} = \frac{3}{2} k\eta^{1/2}$


$\therefore \sigma_e = \left(\frac{3}{2} k\eta^{1/2}\right) \sigma_\eta = \frac{3}{2} k\eta^{3/2} \frac{\sigma_\eta}{\eta} = \frac{3}{2} e \frac{\sigma_\eta}{\eta} \Rightarrow \frac{\sigma_e}{e} = \frac{3}{2} \frac{\sigma_\eta}{\eta}$

Given $\frac{\sigma_\eta}{\eta} = 0.4\%$

$\therefore \frac{\sigma_e}{e} = \frac{3}{2} \times 0.4\% = 0.6\%$. Thus correct answer is option (c).

Q9. For the logic circuit shown in figure, the required input condition (A, B, C) to make the output (X) = 1 is,

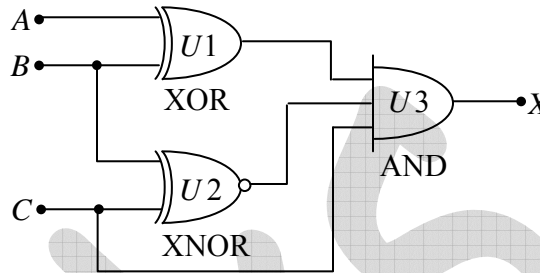- (a) 1,0,1
- (b) 0,0,1
- (c) 1,1,1
- (d) 0,1,1




Ans.: (d)

Solution: XOR is inequality comparator and XNOR is equality comparator. In AND gate output will be high when all the input is 1.

JEST-2016

Q10. It is found that when the resistance R indicated in the figure below is changed from $1\text{ k}\Omega$ to $10\text{ k}\Omega$ the current flowing through the resistance R' does not change. What is the value of the resistor R' ?

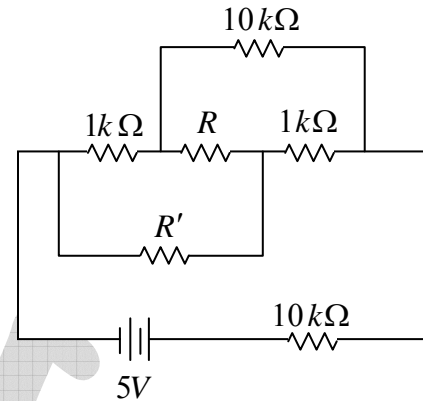
- (a) $5\text{ k}\Omega$
- (b) $100\text{ k}\Omega$
- (c) $10\text{ k}\Omega$
- (d) $1\text{ k}\Omega$



Ans.: (b)

Solution: Apply Wheatstone bridge condition
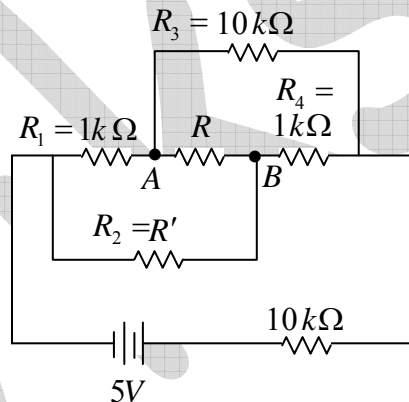
$$\frac{R_1}{R_2} = \frac{R_3}{R_4} \Rightarrow \frac{1}{R'} = \frac{10}{1}$$









Q11. A transistor in common base configuration has ratio of collector current to emitter current β and ratio of collector to base current α . Which of the following is true?

- (a) $\beta = \frac{\alpha}{(\alpha+1)}$
- (b) $\beta = \frac{(\alpha+1)}{\alpha}$
- (c) $\beta = \frac{\alpha}{(\alpha-1)}$
- (d) $\beta = \frac{(\alpha-1)}{\alpha}$

Ans.: (a)

Solution: $\because I_E = I_C + I_B \Rightarrow \frac{I_E}{I_C} = 1 + \frac{I_B}{I_C} \Rightarrow \frac{1}{\beta} = 1 + \frac{1}{\alpha} \Rightarrow \beta = \frac{\alpha}{1+\alpha}$

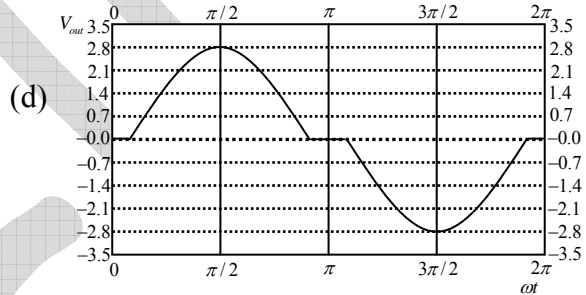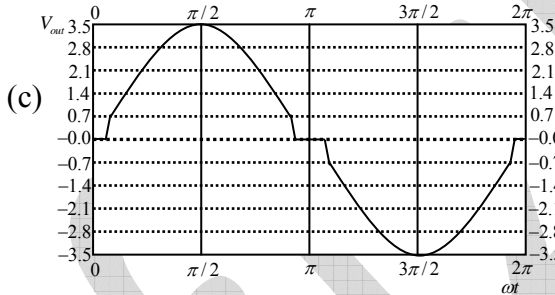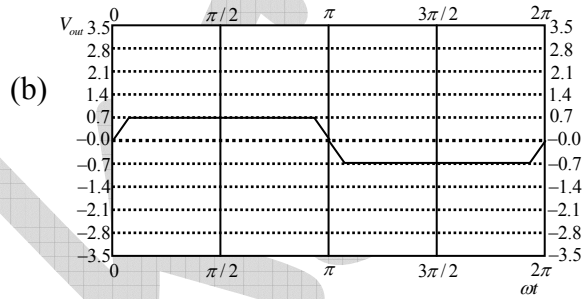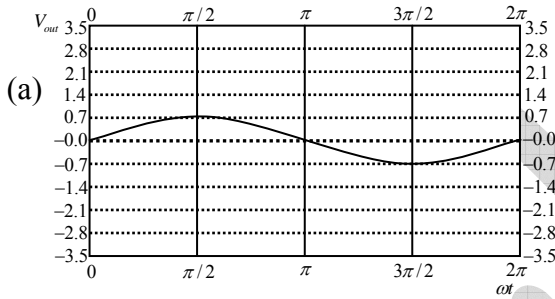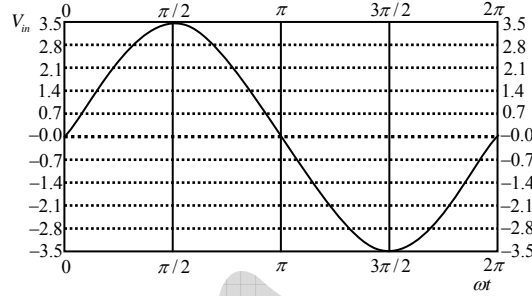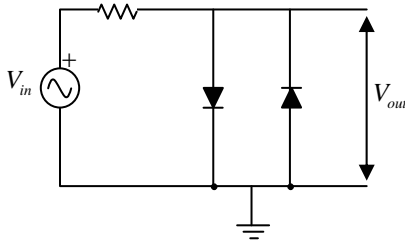Q14. In the following silicon diode circuit ($V_B = 0.7V$), determine the output voltage waveform (V_{out}) for the given input wave.




Ans.: (b)

Solution: Transition voltage $V_T = \pm 0.7V$

When diodes are ON, output voltage will be either $+0.7V$ and $-0.7V$.

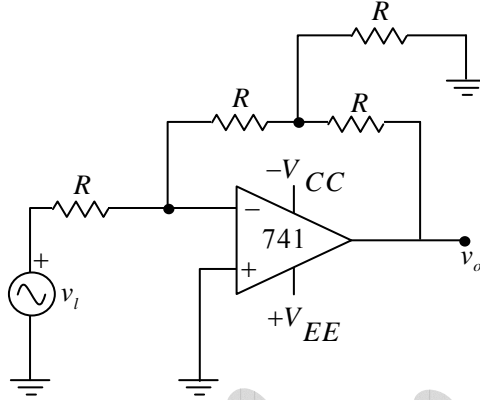Q15. Consider a 741 operational amplifier circuit as shown below, where $V_{CC} = V_{EE} = +15V$ and $R = 2.2k\Omega$. If $v_i = 2mV$, what is the value of v_o with respect to the ground?




- (a) $-1mV$ (b) $-2mV$ (c) $-3mV$ (d) $-4mV$

Ans. : (c)


Solution: Apply KCL;

$$I_1 = I_2 \Rightarrow \frac{v_i - 0}{R} = \frac{0 - v_o}{3R/2}$$
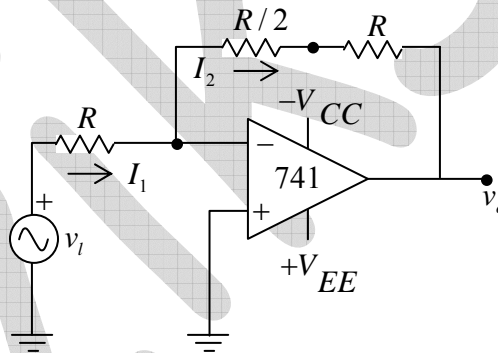
$$\Rightarrow v_o = -\frac{3}{2}v_i = -\frac{3}{2} \times 2 = -3mV$$



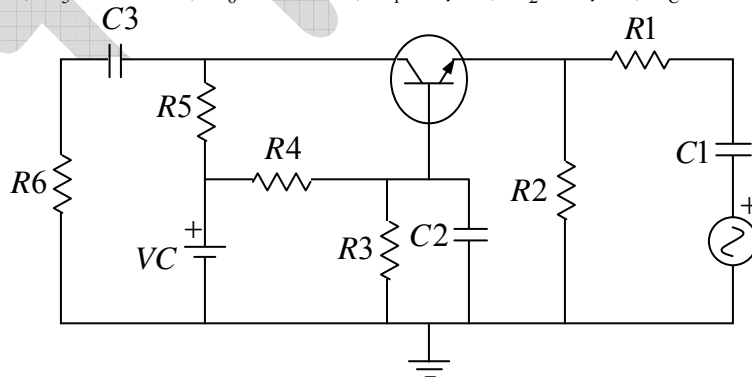
Q16. What is the DC base current (approximated to nearest integer value in μA) for the following $n - p - n$ silicon transistor circuit, given $R_1 = 75\Omega, R_2 = 4.0k\Omega, R_3 = 2.1k\Omega, R_4 = 2.6k\Omega, R_5 = 6.0k\Omega, R_6 = 6.8k\Omega, C_1 = 1\mu F, C_2 = 2\mu F, V_C = +15V, \beta_{dc} = 75$?



- (a) 20 (b) 24 (c) 16 (d) 32

Ans. : (a)

Solution:

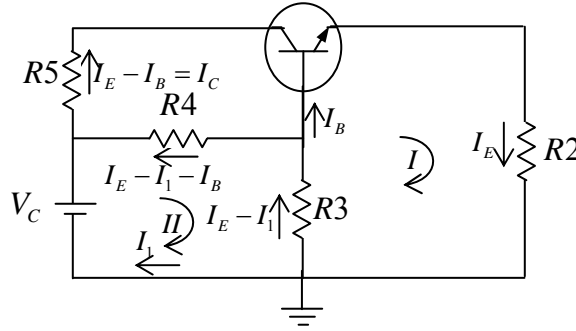

$$\text{Apply KVL in Loop I; } I_E R_2 + (I_E - I_1) R_3 + V_{BE} = 0$$

$$\text{Apply KVL in Loop II; } -V_C - (I_E - I_1 - I_B) R_4 - (I_E - I_1) R_3 = 0$$

$$-V_C - (I_E - I_1) R_4 - (I_E - I_1) R_3 = 0 \Rightarrow I_E - I_1 = -\frac{V_C}{R_3 + R_4}$$

$$\text{From Loop I; } \beta I_B R_2 - \frac{V_C}{R_3 + R_4} R_3 = 0 \Rightarrow I_B = \frac{V_C}{R_3 + R_4} \frac{R_3}{\beta R_2} \quad \because V_{BE} = 0$$

$$\Rightarrow I_B = \frac{15}{2.1 + 2.6} \frac{2.1}{75 \times 4} \approx 21 \mu\text{A}$$