

Electronics

JEST-2012

Ans.: (b)

Solution: Resistance in series is maximum and minimum in parallel combination

$$R_s = 1+1+1+1+\dots N = N$$

$$\frac{1}{R_n} = \frac{1}{1} + \frac{1}{1} + \frac{1}{1} + \frac{1}{1} + \frac{1}{1} \dots = N$$





$$\frac{R_s}{R_p} = N \times N = N^2$$

- Q2. The net charge of an *n*-type semiconductor is
(a) positive (b) zero (c) negative (d) dependent

Ans.: (b)


JEST-2014

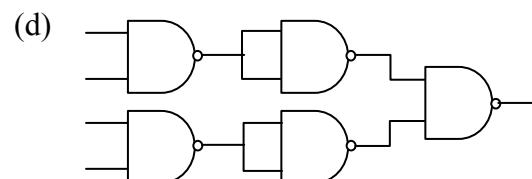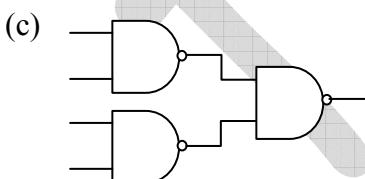
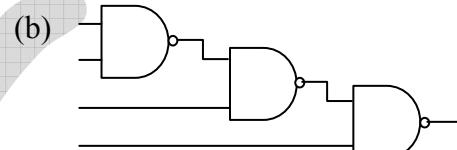
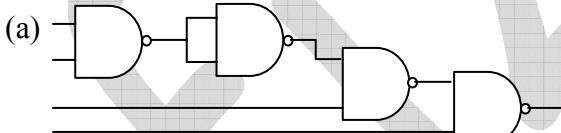
- Q3. Which of the following circuits will act like a 4-input NAND gate?



Ans.: (d)

Solution:

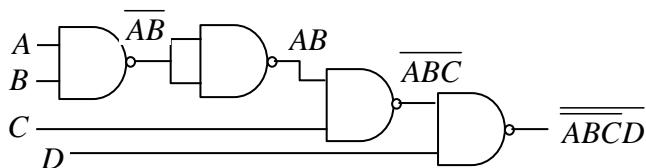

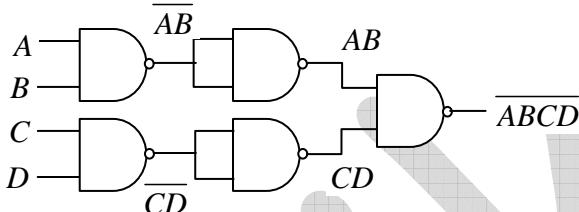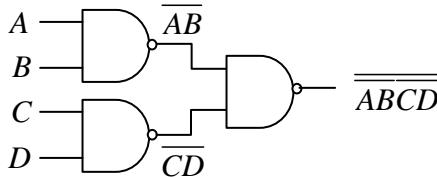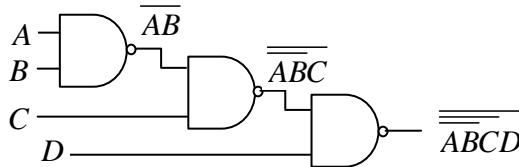

- Q4. The formula for normal strain in a longitudinal bar is given by $\varepsilon = \frac{F}{AE}$, where F is normal force applied, A is cross-sectional area of the bar and E is Young's modulus. If $F = 50 \pm 0.5\text{N}$, $A = 0.2 \pm 0.002\text{m}^2$ and $E = 210 \times 10^9 \pm 1 \times 10^9\text{ Pa}$, the maximum error in the measurement of strain is

(a) 1.0×10^{-12} (b) 2.95×10^{-11} (c) 1.22×10^{-9} (d) 1.19×10^{-9}

Ans.: (b)

$$\text{Solution: } \varepsilon = \frac{F}{AE} \Rightarrow \frac{\Delta\varepsilon}{\varepsilon} = \frac{\Delta F}{F} + \frac{\Delta A}{A} + \frac{\Delta E}{E} = \frac{0.5}{50} + \frac{0.002}{0.2} + \frac{1 \times 10^9}{210 \times 10^9}$$

$$\frac{\Delta\varepsilon}{\varepsilon} = 0.02476 \Rightarrow \Delta\varepsilon = 0.2476 \times \varepsilon = \frac{0.2476 \times 50}{0.2 \times 210 \times 10^9} = 2.95 \times 10^{-11}$$

- Q5. A 100 ohms resistor carrying current of 1 Amp is maintained at a constant temperature of 30°C by a heat bath. What is the rate of entropy increase of the resistor?

(a) 3.3 Joules/K/sec (b) 6.6 Joules/K/sec
 (c) 0.33 Joules/K/sec (d) None of the above


Ans.: (c)

$$\text{Solution: } W = qV \Rightarrow W = itV \Rightarrow W = i^2 R t. \text{ Now, } \frac{\partial W}{\partial T} = \frac{i^2 R t}{T} = \frac{1 \times 100}{30 + 273} = 0.33$$

JEST-2015

- Q6. What is the voltage at the output of the following operational amplifier circuit. [See in the figure]?

- (a) 1V
- (b) 1mV
- (c) 1 μ V
- (d) 1nV

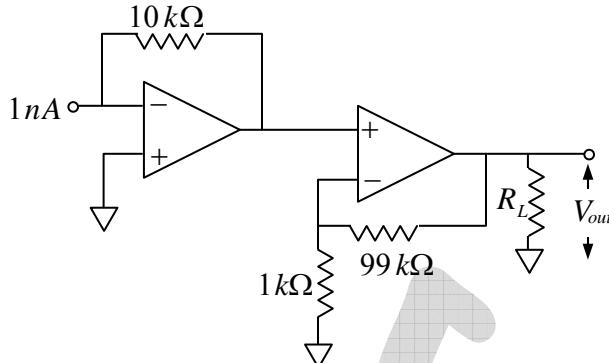

Ans.: (b)

Solution: Output of first Op-Amp $v_{o1} = -(10 \times 10^3)(1 \times 10^{-9}) = -10^{-5}$ volt

$$\text{Output of first Op-Amp } v_{out} = \left(1 + \frac{99}{1}\right) \times 10^{-5} = 10^{-3} \text{ volts} = 1 \text{ mV}$$

- Q7. The reference voltage of an analog to digital converter is 1 V. The smallest voltage step that the converter can record using a 12-bit converter is,

- (a) 0.24V
- (b) 0.24mV
- (c) 0.24 μ V
- (d) 0.24nV

Ans.: (b)

Solution: Smallest voltage step = $\frac{1}{2^{12}-1} \approx 0.24 \text{ mV}$

- Q8. In Millikan's oil drop experiment the electronic charge e could be written as $k\eta^{1.5}$, where k is a function of all experimental parameters with negligible error. If the viscosity of air η is taken to be 0.4% lower than the actual value, what would be the error in the calculated value of e ?

- (a) 1.5%
- (b) 0.7%
- (c) 0.6%
- (d) 0.4%

Ans.: (d)

Solution: Electronic charge is proportional to the viscosity i.e. $e = k\eta^{1.5} = k\eta^{3/2}$

Now error in the measurement of charge is $\sigma_e^2 = \left(\frac{\partial e}{\partial \eta}\right)^2 \sigma_\eta^2$

$$\Rightarrow \sigma_e = \left(\frac{\partial e}{\partial \eta}\right) \sigma_\eta, \text{ where } \frac{\partial e}{\partial \eta} = \frac{3}{2} k \eta^{1/2}$$

$$\therefore \sigma_e = \left(\frac{3}{2} k \eta^{1/2}\right) \sigma_\eta = \frac{3}{2} k \eta^{3/2} \frac{\sigma_\eta}{\eta} = \frac{3}{2} e \frac{\sigma_\eta}{\eta} \Rightarrow \frac{\sigma_e}{e} = \frac{3}{2} \frac{\sigma_\eta}{\eta}$$

Given $\frac{\sigma_\eta}{\eta} = 0.4\%$

$$\therefore \frac{\sigma_e}{e} = \frac{3}{2} \times 0.4\% = 0.6\%. \text{ Thus correct answer is option (c).}$$

Q9. For the logic circuit shown in figure, the required input condition (A, B, C) to make the output $(X) = 1$ is,

- (a) 1,0,1
- (b) 0,0,1
- (c) 1,1,1
- (d) 0,1,1

Ans.: (d)

Solution: XOR is inequality comparator and XNOR is equality comparator. In AND gate output will be high when all the input is 1.

JEST-2016



Q10. It is found that when the resistance R indicated in the figure below is changed from $1 k\Omega$ to $10 k\Omega$ the current flowing through the resistance R' does not change. What is the value of the resistor R' ?

- (a) $5 k\Omega$
- (b) $100 k\Omega$
- (c) $10 k\Omega$
- (d) $1 k\Omega$

Ans.: (b)

Solution: Apply Wheatstone bridge condition
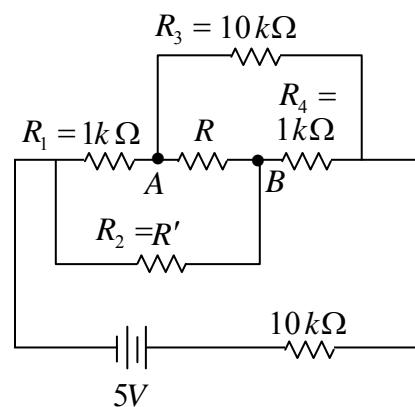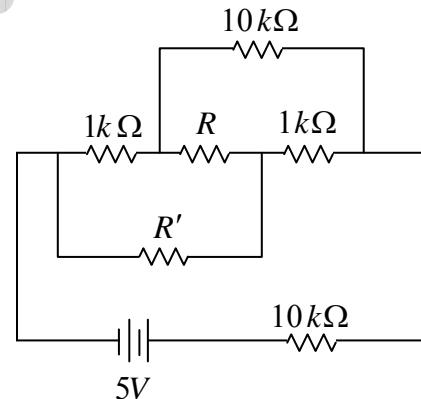
$$\frac{R_1}{R_2} = \frac{R_3}{R_4} \Rightarrow \frac{1}{R'} = \frac{10}{1}$$



Q11. A transistor in common base configuration has ratio of collector current to emitter current β and ratio of collector to base current α . Which of the following is true?

- (a) $\beta = \frac{\alpha}{(\alpha+1)}$ (b) $\beta = \frac{(\alpha+1)}{\alpha}$ (c) $\beta = \frac{\alpha}{(\alpha-1)}$ (d) $\beta = \frac{(\alpha-1)}{\alpha}$

Ans.: (a)

Solution: $\because I_E = I_C + I_B \Rightarrow \frac{I_E}{I_C} = 1 + \frac{I_B}{I_C} \Rightarrow \frac{1}{\beta} = 1 + \frac{1}{\alpha} \Rightarrow \beta = \frac{\alpha}{1+\alpha}$

JEST - 2017



Q12. Consider the circuit shown in the figure where $R_1 = 2.07 k\Omega$ and $R_2 = 1.93 k\Omega$. Current source I delivers $10mA$ current. The potential across the diode D is $0.7V$. What is the potential at A ?

- (a) $10.35V$ (b) $9.65V$
 (c) $19.30V$ (d) $4.83V$


Ans. : (b)

Solution: Apply KVL in loop I
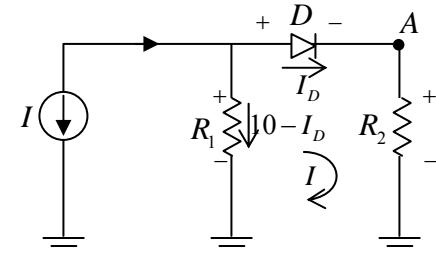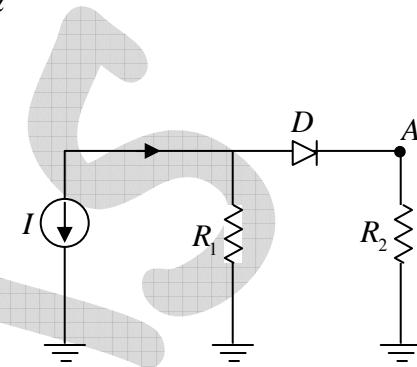
$$\begin{aligned} 0.7 + I_D R_2 - (10 - I_D) R_1 &= 0 \\ \Rightarrow 0.7 + I_D \times 1.93 - (10 - I_D) \times 2.07 &= 0 \\ \Rightarrow I_D = 5mA \Rightarrow V_A = I_D R_2 &= 5mA \times 1.93 k\Omega = 9.65V \end{aligned}$$



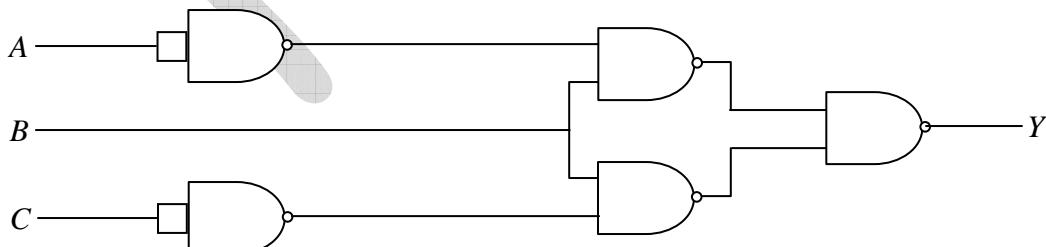
Q13. What is Y for the circuit shown below?









- (a) $Y = \overline{(A + \bar{B})(\bar{B} + C)}$ (b) $Y = \overline{(A + \bar{B})(B + C)}$
 (c) $Y = \overline{(\bar{A} + B)(\bar{B} + C)}$ (d) $Y = \overline{(A + B)(\bar{B} + C)}$

Ans.: (a)

Solution:

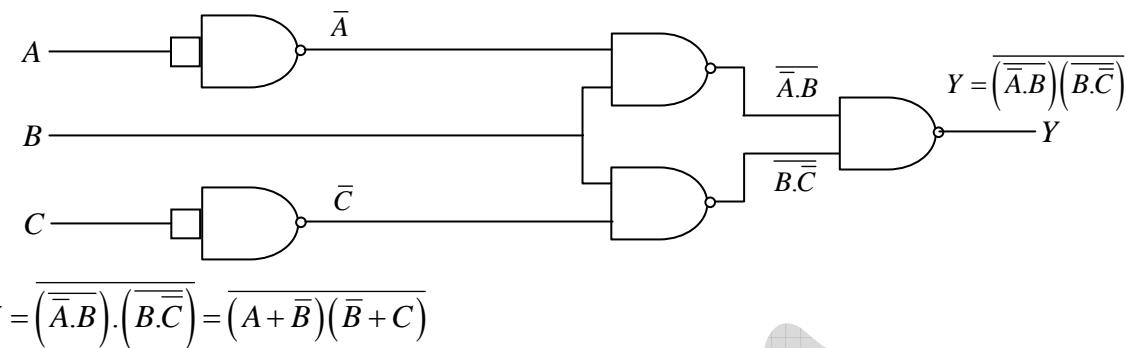

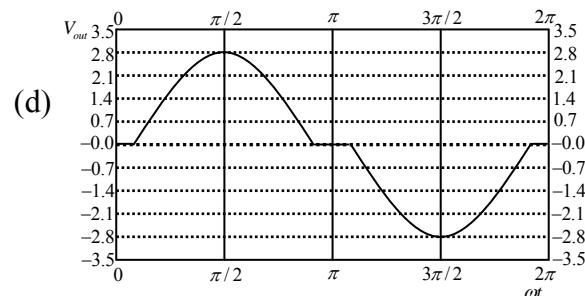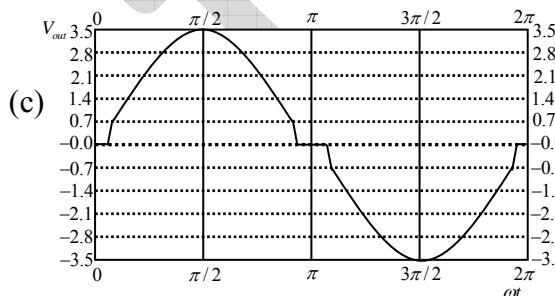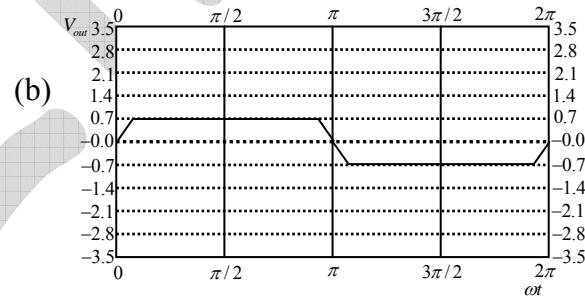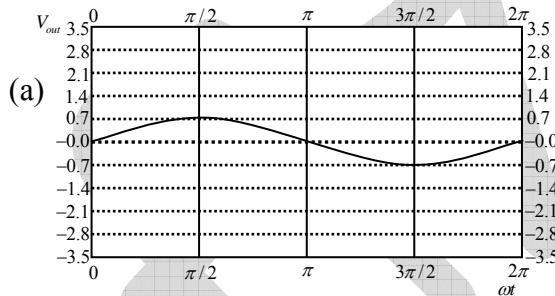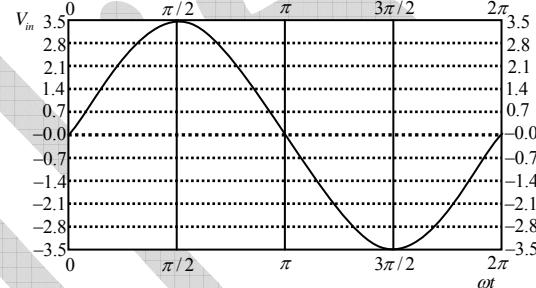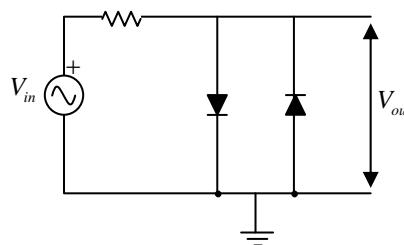Q14. In the following silicon diode circuit ($V_B = 0.7V$), determine the output voltage waveform (V_{out}) for the given input wave.




Ans.: (b)

Solution: Transition voltage $V_T = \pm 0.7V$

When diodes are ON, output voltage will be either $+0.7V$ and $-0.7V$.

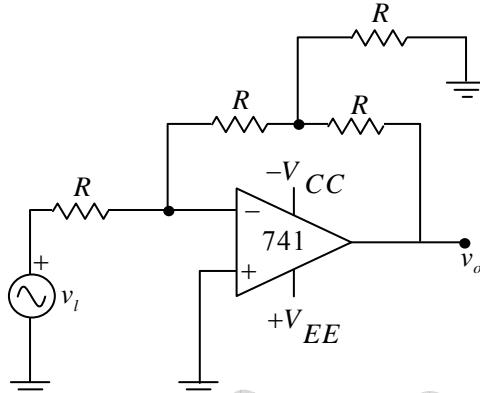- Q15. Consider a 741 operational amplifier circuit as shown below, where $V_{CC} = V_{EE} = +15V$ and $R = 2.2 k\Omega$. If $v_i = 2mV$, what is the value of v_o with respect to the ground?



(a) $-1mV$

(b) $-2mV$

(c) $-3mV$


(d) $-4mV$

Ans. : (c)


Solution: Apply KCL;

$$I_1 = I_2 \Rightarrow \frac{v_i - 0}{R} = \frac{0 - v_o}{3R/2}$$
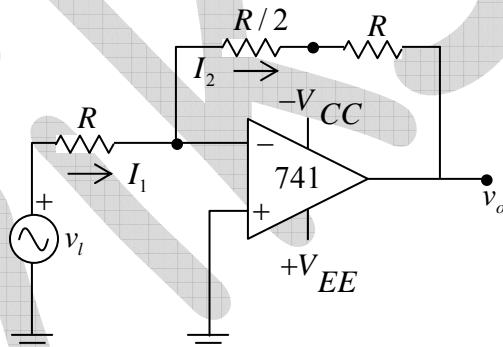
$$\Rightarrow v_o = -\frac{3}{2}v_i = -\frac{3}{2} \times 2 = -3mV$$



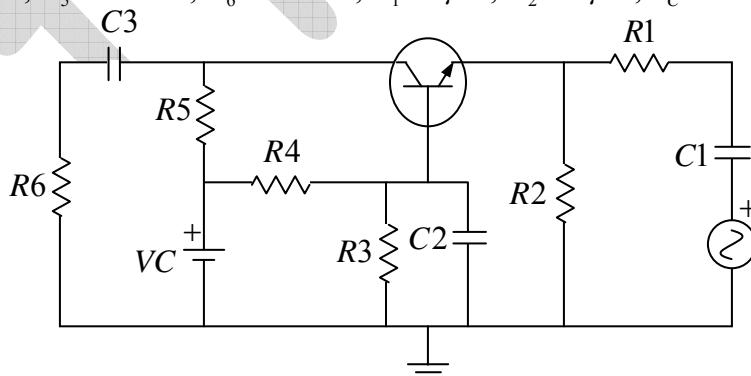- Q16. What is the DC base current (approximated to nearest integer value in μA) for the following $n-p-n$ silicon transistor circuit, given $R_1=75\Omega$, $R_2=4.0 k\Omega$, $R_3=2.1 k\Omega$, $R_4=2.6 k\Omega$, $R_5=6.0 k\Omega$, $R_6=6.8 k\Omega$, $C_1=1\mu F$, $C_2=2\mu F$, $V_C=+15V$, $\beta_{dc}=75$?



(a) 20


(b) 24

(c) 16

(d) 32

Ans. : (a)

Solution:

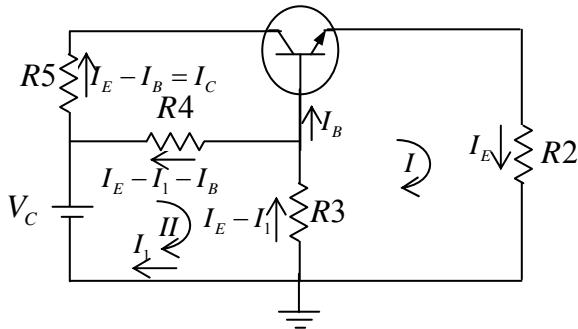

$$\text{Apply KVL in Loop I; } I_E R_2 + (I_E - I_1) R_3 + V_{BE} = 0$$

$$\text{Apply KVL in Loop II; } -V_C - (I_E - I_1 - I_B) R_4 - (I_E - I_1) R_3 = 0$$

$$-V_C - (I_E - I_1) R_4 - (I_E - I_1) R_3 = 0 \Rightarrow I_E - I_1 = -\frac{V_C}{R_3 + R_4}$$

$$\text{From Loop I; } \beta I_B R_2 - \frac{V_C}{R_3 + R_4} R_3 = 0 \Rightarrow I_B = \frac{V_C}{R_3 + R_4} \frac{R_3}{\beta R_2} \quad \because V_{BE} = 0$$

$$\Rightarrow I_B = \frac{15}{2.1+2.6} \frac{2.1}{75 \times 4} \approx 21 \mu A$$

JEST-2018

- Q17. A Germanium diode is operated at a temperature of 27 degree C. The diode terminal voltage is 0.3 V when the forward current is 10 mA. What is the forward current (in mA) if the terminal voltage is 0.4 V?

- (a) 477.3 (b) 577.3 (c) 47.73 (d) 57.73


Ans. : (a)

Solution: $I = I_0 (e^{V/V_T} - 1) \approx I_0 e^{V/V_T}$ where $V_T = \frac{kT}{e} = 0.026V$

$$\Rightarrow 10mA = I_0 e^{0.3/0.026} = I_0 e^{11.54} \Rightarrow I_0 = \frac{10}{102744} mA$$

$$\text{Thus, } I = I_0 e^{0.4/0.026} = \frac{10}{102744} \times 4876800 mA \approx 474.6 mA$$

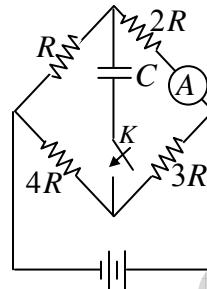- Q18. In the circuit shown below, the capacitor is initially uncharged. Immediately after the key K is closed, the reading in the ammeter is 27 mA .



What will the reading (in mA) be a long time later?

Ans. : 30

Solution: Immediately after the key K is closed, capacitor is short circuited. Using KCL

$$I_1 = \frac{3R}{5R} \times I = 27 \text{ mA} \Rightarrow I = 45 \text{ mA}.$$

$$R_{eq} = \frac{2R \times 3R}{5R} + \frac{R \times 4R}{5R} = 2R$$

$$\text{Thus } V = IR_{eq} = 90R$$



After long time, capacitor is open circuited.

Using KCL

$$R_{eq} = \frac{3R \times 7R}{10R} = \frac{21}{10}R$$

$$I' = \frac{V}{R_{eq}} = \frac{90R}{21R/10} = \frac{300}{7} \text{ mA}$$
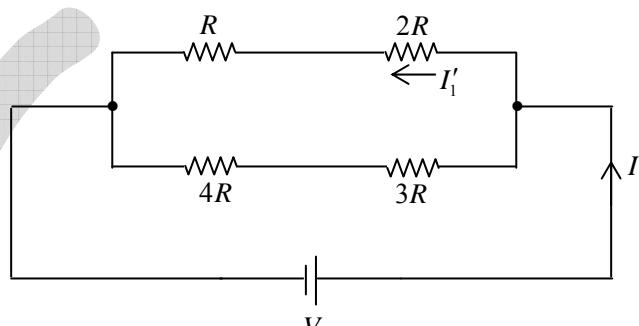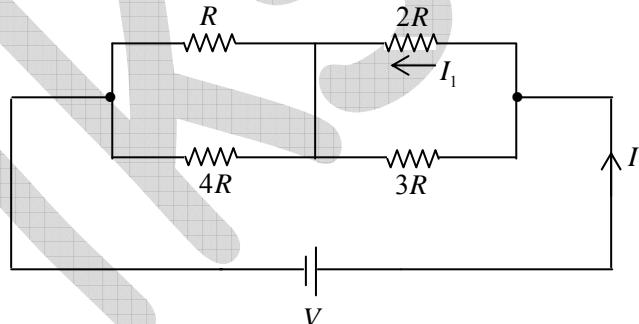
$$I'_1 = \frac{7R}{10R} \times \frac{300}{7} \text{ mA} = 30 \text{ mA}.$$




Q19. Consider the transistor circuit shown in the figure.

Assume $V_{BEQ} = 0.7 \text{ V}$, $V_{BB} = 6\text{V}$ and the leakage current is negligible. What is the required value of R_B in kilo-ohms if the base current is to be $4 \mu\text{A}$?

Ans. : 1325


Solution: Apply LVL in input section
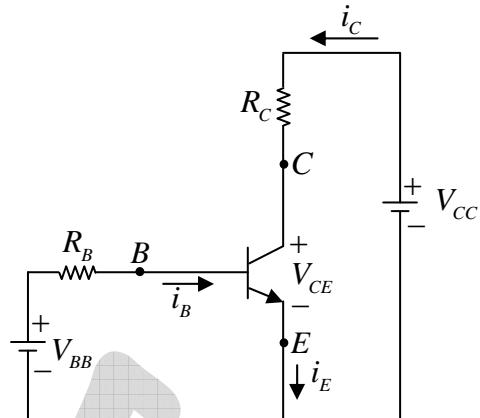
$$\begin{aligned} -V_{BB} + I_B R_B + V_{BE} &= 0 \\ \Rightarrow R_B &= \frac{V_{BB} - V_{BE}}{I_B} = \frac{6V - 0.7V}{4 \times 10^{-3} \text{ mA}} = 1325 \text{ k}\Omega \end{aligned}$$



JEST-2019

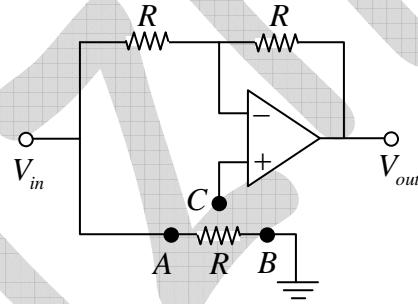Q20. Analyse the ideal op-amp circuit in the figure. Which one of the following statements is true about the output voltage V_{out} , when terminal ‘C’ is connected to point ‘A’ and then to point ‘B’?



- (a) $V_{out} = V_{in}$ and $V_{out} = -V_{in}$ when ‘C’ is connected to ‘A’ and ‘B’, respectively
- (b) $V_{out} = -V_{in}$ and $V_{out} = V_{in}$ when ‘C’ is connected to ‘A’ and ‘B’, respectively
- (c) $V_{out} = -V_{in}$ when ‘C’ is connected to either ‘A’ or ‘B’
- (d) $V_{out} = V_{in}$ when ‘C’ is connected to either ‘A’ or ‘B’

Ans. : (a)


Solution: When terminal ‘C’ is connected to point ‘A’

$$V_{out} = \left(1 + \frac{1}{1}\right)V_{in} - \frac{1}{1}V_{in} = V_{in}$$

When terminal ‘C’ is connected to point ‘B’

$$V_{out} = -\frac{1}{1}V_{in} = -V_{in}$$

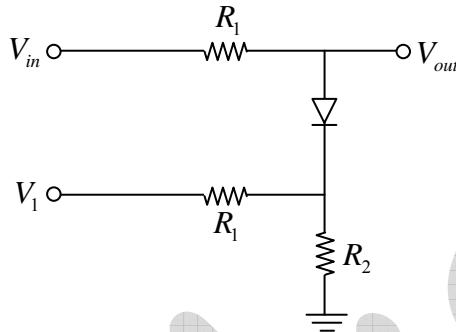- Q21. The circuit given below is fed by a sinusoidal voltage $V_{in} = V_0 \sin \omega t$. Assume that the cut-in voltage of the diode is 0.7 volts and V_1 is a positive dc voltage smaller than V_0 . Which one of the following statements is true about V_{out} ?



- (a) Positive part of V_{out} is restricted to a maximum voltage of $0.7 + \frac{R_2}{R_1 + R_2} V_1$
- (b) Negative part of V_{out} is restricted to a maximum voltage of $0.7 + \frac{R_2}{R_1 + R_2} V_1$
- (c) Positive part of V_{out} is restricted to a maximum voltage of $0.7 + \frac{R_1}{R_1 + R_2} V_1$
- (d) Negative part of V_{out} is restricted to a maximum voltage of $0.7 + \frac{R_1}{R_1 + R_2} V_1$

Ans. : (a)

Solution: Reference voltage $V_R = \frac{R_2}{R_1 + R_2} V_1$ and diode will be ON when $V_{in} > \left(0.7 + \frac{R_2}{R_1 + R_2} V_1 \right)$.